

CS223 Laboratory Assignment 1

Digital Circuits: Logic to Gates

Lab dates and times:

Section 1:	07.10.2019	Monday	08:40-12:25
Section 2:	08.10.2019	Tuesday	08:40-12:25
Section 3:	07.10.2019	Monday	13:40-17:25
Section 4:	08.10.2019	Tuesday	13:40-17:25
Section 5:	10.10.2019	Thursday	08:40-12:25
Section 6:	11.10.2019	Friday	08:40-12:25

Location: EA Z04 (in the EA building, straight ahead past the elevators)

Groups: Each student will do the lab individually. Group size = 1

Preliminary Work (20 points)

(You should do this part before coming to lab).

Physical gates are built out of transistors, and require physical signals that use correct voltage levels for inputs and produce physical signals that use correct voltage levels for outputs. To work correctly, the transistor circuits that comprise a gate must have connections to a voltage supply and to ground. For example, in the case of 74-series logic circuits used in this lab, the supply voltage (V_{cc}) must be 5 volts. In these integrated circuit packages, several gates are contained. Search Google specifying that gate number and its function (e.g. "7486 XOR gate") for pin connection diagrams, such as the pin diagram shown in Figure 1. You must have the pin diagrams for each gate you want to use, in order to do the following tasks. You can find pinout of rest of 74-series gates here: <http://www.qsl.net/on7pc/datasheet/ttl7400/7400family.pdf>. Other gates you need today are: 7408 quad 2-input AND, 7432 quad 2-input OR and 7404 hex 1-input INVERTER.

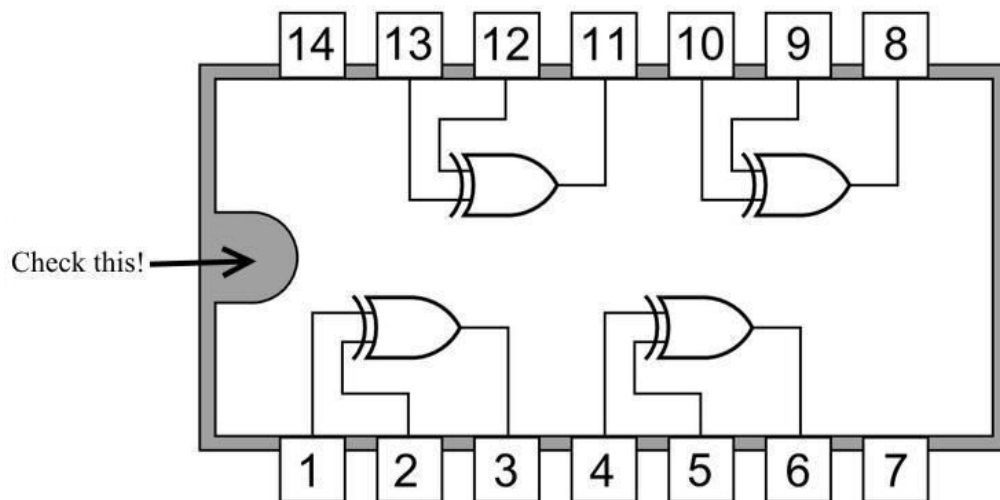


Figure 1: 7486 Quad 2-input XOR gate

First, read the document posted in Unilica for CS223 labs: “Circuit Schematic versus Logic Diagram”. Then, using the logic diagram in Figure 2 (below) as a starting point, draw a circuit schematic of the digital circuit "you will build. This should include **pin numbers** marked on the inputs and outputs of all the gates, **part numbers** (IC's code) of the IC package marked on each gate, plus **power and ground connections** marked on the side of the drawing. Do this for all circuits in Figure 2 and Figure 3. Make sure that you put 4 circuit schematics which are, half adder, half subtractor, full adder and full subtractor.

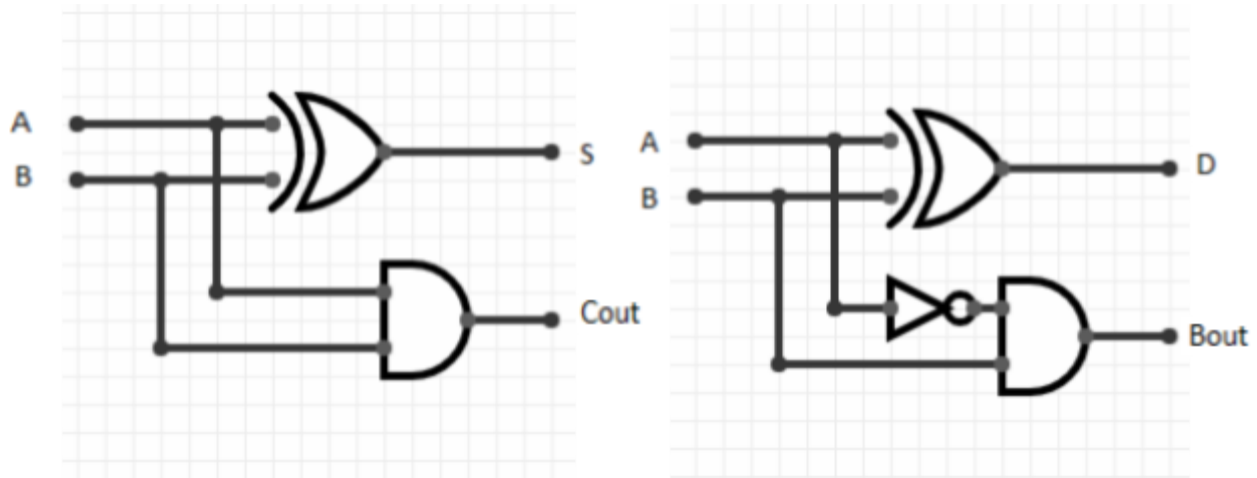


Figure 2: Half Adder(left) & Subtractor(right)

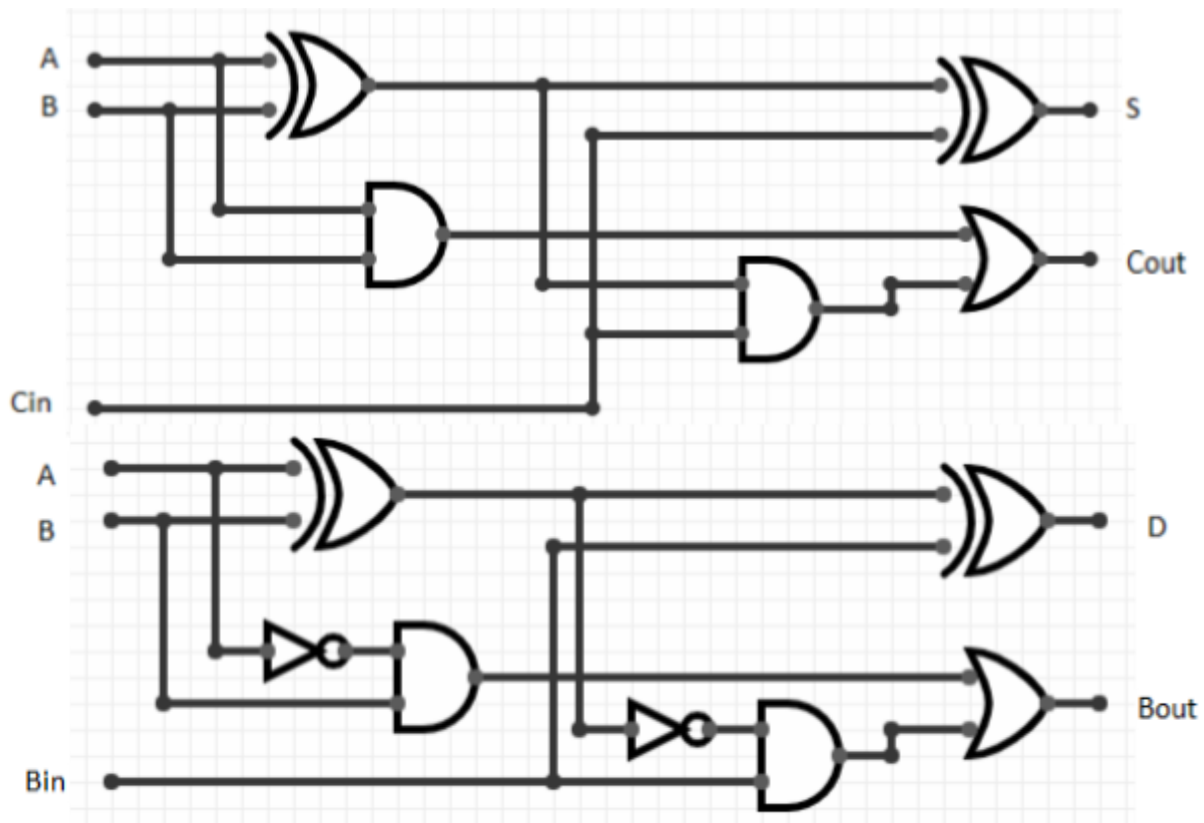


Figure 3: Full Adder(above) & Subtractor(below)

On the Figure 2 and Figure 3, A and B indicate standard input bits; S, D, Bin, Cin, Bout and Cout represents Sum, Difference, Borrow-in, Carry-in, Borrow-out and Carry-out respectively. If you want to understand deeply what these bits do, check Figure 5.

Prepare preliminary report, on top each page you should provide the following information:

Section No

Lab No

Your Full Name

Bilkent ID

Preliminary report should contain 4 circuit schematics mentioned before. Also it is a good idea to take a copy for yourself to use in the lab because the preliminary reports will be collected before the start of lab.

Recommendations

1. In CS223 labs, you build circuits by ICs and later by FPGA. It is better to obey some simple rules to avoid damaging electronic parts or confusing yourself with debugging your circuit.
2. Avoid touching IC or FPGA pins directly by your hand. Static electricity in your body can damage them permanently.
3. The white board which you setup your circuit on it, is called “breadboard”. Search the internet and find out how its pins are connected internally.
4. Postpone connecting power pins (Vcc and ground) to last step. Check circuit connections and if everything seems ok then connect power pins.
5. For easier debugging of circuits, always follow a wire color convention. For example, always use black or white wire for ground and red wire for Vcc.
6. If LED’s light is weak, or if the IC’s package is very hot (you can touch plastic part) you have a problem in the power pin connections (short circuit, connecting Vcc wire to ground pin,...).

Part 1: Practice with Logic Gates (35 points)

- 1) Ask the TA or Tutor to come and check your first schematic (which is converted from Figure 2). *Do not proceed to the next step until* you have verified that your circuit schematic is correct, and the TA or Tutor has approved it.
- 2) Using your circuit schematic for half adder/subtractor , build the circuit step-by-step, following the **Digital Circuit Suggestions** given in Unilica and recommendations in page-2. Connect the inputs to switches on the logic board. Connect the outputs of your logic circuit to LEDs on the logic board. Don't forget to connect +VCC power and GND ground to the VCC and GND pins on both IC packages.
- 3) Make a test probe by connecting another LED on the logic board to one end of a long wire, whose other end will be used to touch circuit points and “see” the logic values. A full voltage level ~5 V will cause the LED to shine brightly; a 0 V level will not light up the LED. A low light output from the LED means that the voltage being sensed is in between logic 0 and logic 1, meaning something is WRONG with your circuit.
- 4) Now draw the truth table for the 2-input 2-output logic circuits that you have made, and fill in the left-hand (input) side in standard binary counting order. For each row, apply the input combinations by adjusting the switches, and measure the output. Use this information to complete the truth table, filling in the right-hand (output) side.
- 5) Compare your measured truth table that you just obtained from the circuit, with the below one. If there are no discrepancies, then it means that your logic circuit has worked as predicted. Ask the TA or Tutor to come and verify this. When the TA or Tutor has checked your circuit, you are done with this part. Note that there is no restriction about showing both circuits (half adder and half subtractor) at the same time, or one by one. Yet we suggest you to show circuits one by one because otherwise you may stuck on simple error with complex circuit.

Input		Output	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Input		Output	
A	B	D	B _{out}
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Figure 4: Half Adder & Subtractor Truth Tables

Part 2: Understanding and Building a Full Adder & Subtractor (45 points)

- 1) In part 1 you implemented half adder & subtractor. Here you will do the same for full-adder & subtractor, a circuit for two bits(represented as A and B) and carry-in/borrow-in bit (represented as C) . As you did in part 1, ask the TA or Tutor to come and check your second schematic (which is converted from Figure 3). *Do not proceed to the next step until* you have verified that your circuit schematic is correct, and the TA or Tutor has approved it.
- 2) Using your circuit schematic, build the circuit, following the Digital Circuit Suggestions given in Unilica. Connect the inputs to switches on the logic board. Connect the outputs of your logic circuit to LEDs on the logic board. Don't forget to connect +VCC power and GND ground to the VCC and GND pins on all the IC packages.
- 3) As you did in Part 1, test and verify that your built circuit is working as a full adder & subtractor, correctly producing outputs for each combination inputs and draw a truth table. When it is debugged and working correctly, ask the TA or Tutor to come and verify this. When the TA or Tutor has checked your circuit, you are done with this part. Again you can show both functionality at the same time or one by one. Keep in mind, this time showing both functionality at the same time will be more challenging because of the lack of wires or gates.

Inputs			Full Adder		Full Subtractor	
A	B	C	Sum	Carry	Diff.	Borrow
0	0	0	0	0	0	0
0	0	1	1	0	1	1
0	1	0	1	0	1	1
0	1	1	0	1	0	1
1	0	0	1	0	1	0
1	0	1	0	1	0	0
1	1	0	0	1	0	0
1	1	1	1	1	1	1

Figure 5: Full Adder & Subtractor Truth Tables

Clean Up

- 1) Clean up your lab station, and return all the parts, wires, the Beti trainer board, etc. Leave your lab workstation for others the way you would like to find it.
- 2) CONGRATULATIONS! You are finished with Lab #1 and are one step closer to becoming a computer engineer.

NOTES

--Advance work on this lab, and all labs, is strongly suggested.

--Be sure to read and follow the Policies for CS223 labs, posted in Unilica.

LAB POLICIES

1. There are three computers in each row in the lab. Don't use middle computers, unless you are allowed by lab coordinator.
2. You borrow a lab-board containing the development board, connectors, etc. in the beginning. The lab coordinator takes your signature. When you are done, return it to his/her, otherwise you will be responsible and lose points.
3. Each lab-board has a number. You must always use the same board throughout the semester.
4. You must be in the lab, working on the lab, from the time lab starts until you finish and leave. (bathroom and snack breaks are the exception to this rule). Absence from the lab, at any time, is counted as an absence from the whole lab that day.
5. No cell phone usage during lab. Tell friends not to call during the lab hours--you are busy learning how digital circuits work!
6. Internet usage is permitted only to lab-related technical sites. No Facebook, Twitter, email, news, video games, etc--you are busy learning how digital circuits work!
7. If you come to the lab later than 20 minutes, you will lose that session completely.
8. When you are done, DO NOT return IC parts into the IC boxes where you've taken them first.

Just put them inside your Lab-board box. Lab coordinator will check and return them later.